

## GENERATOR SOLUTIONS AND TEST

### PROBLEM 5-1 (continued)

Then:

$$\begin{aligned}V_a &= \frac{11,000\angle 0^\circ}{\sqrt{3}} + (656)\angle \cos^{-1} 0.8 (10)\angle +90^\circ \\&= 6,351 + (656)(0.8 - j0.6)(j10) = 6,351 + j5,248 + 3,936 \\&= 10,287 + j5,248 = 11.548\angle 27.02^\circ \text{ kV} \leftarrow \boxed{\text{Answer to (a)}}\end{aligned}$$

Determine the excitation voltage at a 1.0 power factor and 10 MW.

$$I_L = \frac{10^7}{\sqrt{3}(11)(10^3)} = 525 \text{ A}$$

Then:

$$V_a = 6,351 + 525(1)(j10) = 6,351 + j5,250 = 8.239\angle 39.6^\circ \text{ kV} \leftarrow \boxed{\text{Answer to (b)}}$$

Determine the excitation voltage at a 0.8 power factor leading and 10 MW.

$$I_p = 656 \text{ A}$$

Then:

$$\begin{aligned}V_a &= 6,351 + 656(0.8 + j0.6)(j10) = 6,351 + j5,248 - 3,936 \\&= 5.777\angle 65.3^\circ \text{ kV} \leftarrow \boxed{\text{Answer to (c)}}\end{aligned}$$

Determine the maximum power under the same conditions.

Since:

$$P_{3\phi} = \frac{|V_g| |V_m| \sin \delta}{X}$$

where:  $|V_g|$  and  $|V_m|$  are line-to-line voltage;  $P = 3\phi \text{ W}$ ; and  $\delta$  is the angle between  $|V_g|$  and  $|V_m|$ .